

LOW POWER DIGITAL EQUALIZATION FOR HIGH SPEED SERDES

Masum Hossain


University of Alberta



Outline

- **Why ADC-Based receiver?**
- **Challenges in ADC-based receiver**
- **ADC-DSP based Receiver**
 - Reducing impact of Quantization Noise
 - Variable Resolution ADC
 - low-latency high-resolution TDC-based timing recovery
 - Implemented Prototype and Measured Results

Conventional mixed-signal Link

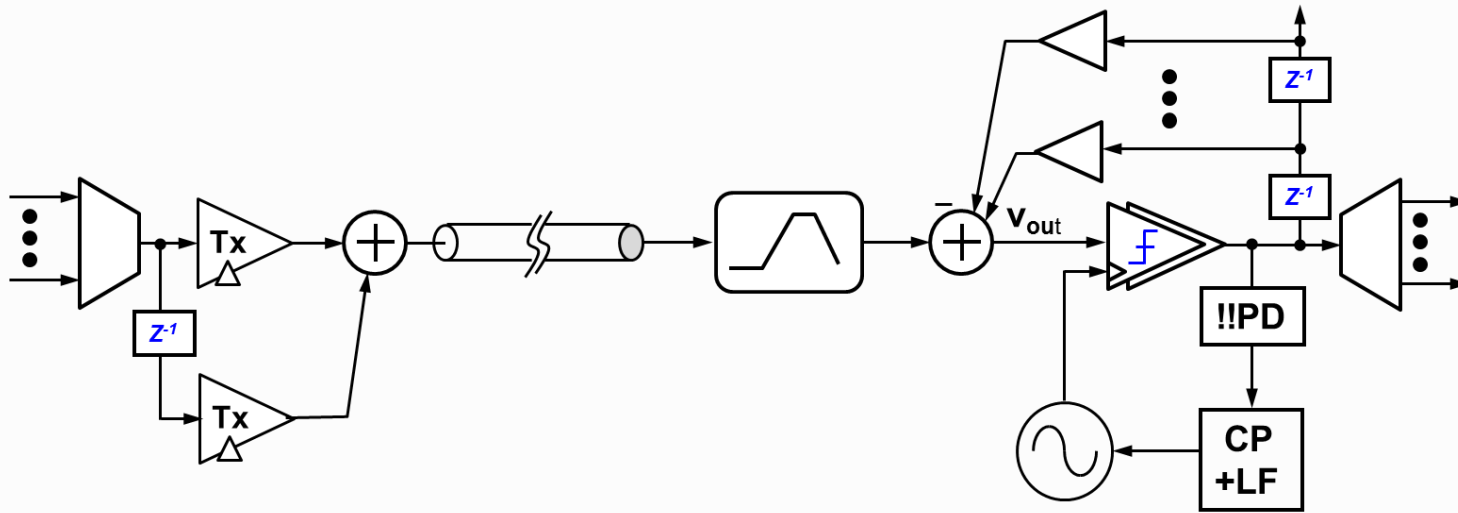

Tx FIR Filter:

- Peak power constrained
- Limited by supply voltage

Peaking equalizer:

- Analog - does not scale well
- Limited by supply voltage
- PVT variation


Decision Feedback Eq.:

- Latency constrained
- Difficult for multilevel signaling

Existing equalization strategy does not scale well with technology, channel loss and data rate

Mixed-signal vs ADC-based Link

ADC-based high speed Link

 

Benefits of DSP-based equalization:


- Scales well with technology
- Frequency response can be well controlled
- Can equalize both pre and post cursors

Challenges of DSP-based equalization:


- ADC-DSP is power hungry.
- Higher loop latency make timing recovery difficult

PAM-4 Digital Receiver Architecture

- Variable Resolution
- Predictive ADC


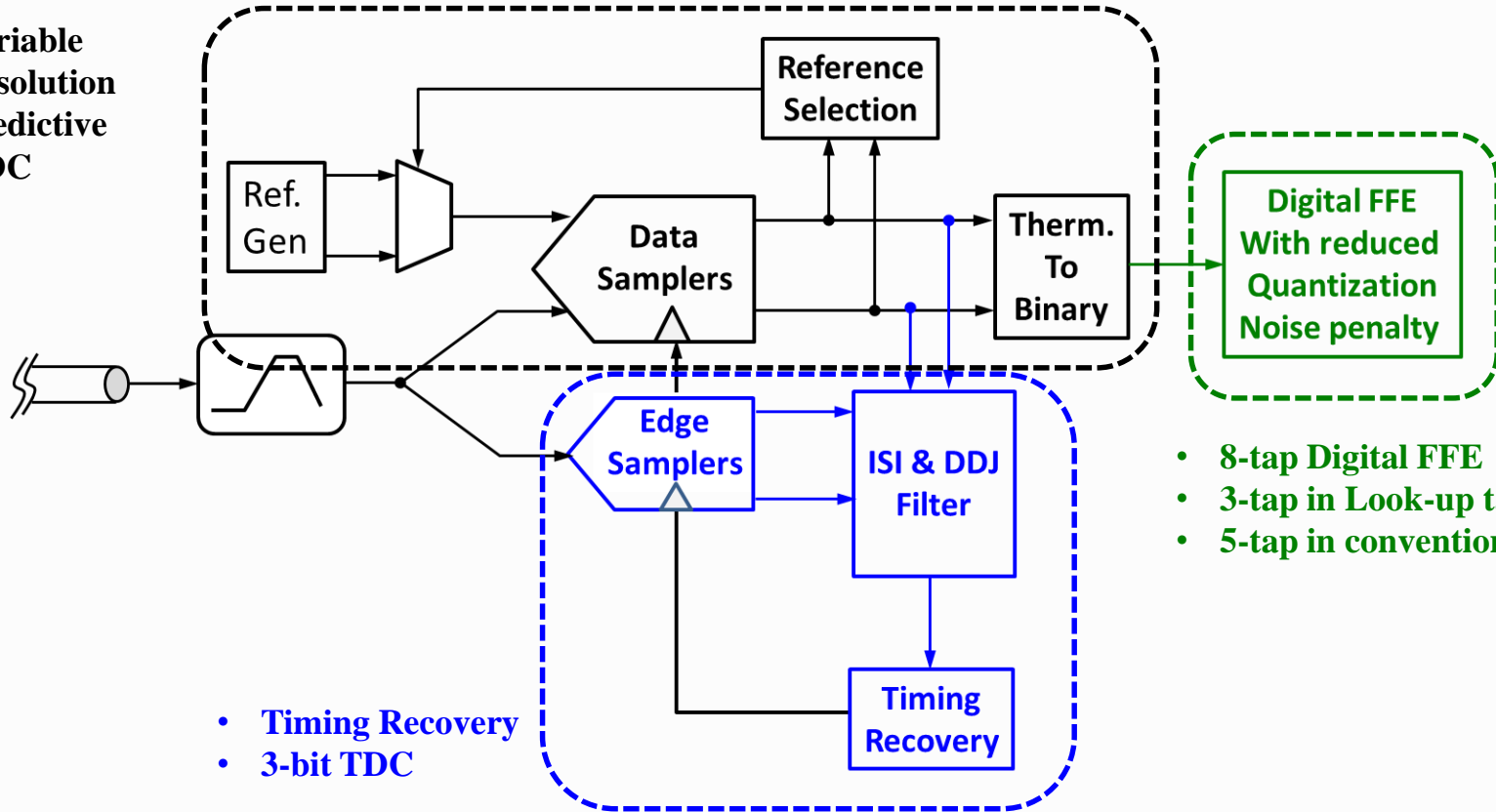


Variable Resolution ADC - 12 dB loss

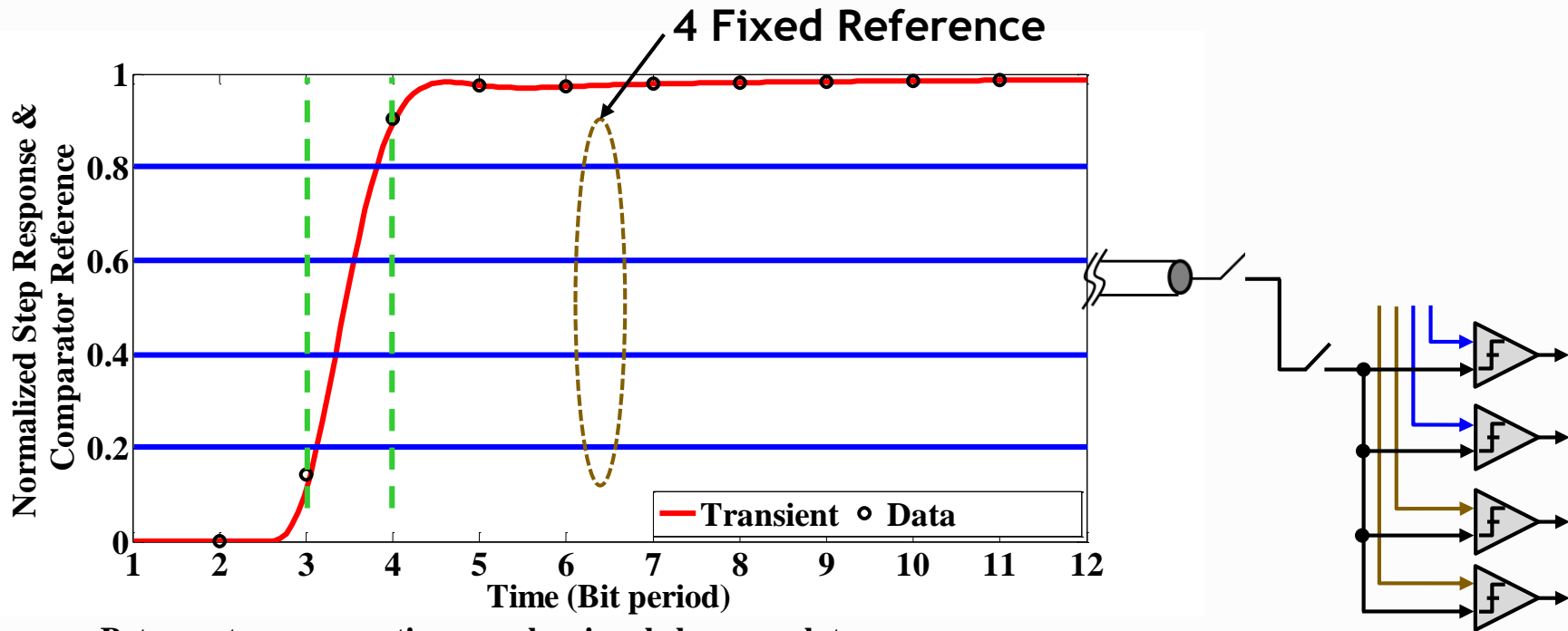


- Between two consecutive samples signal changes a lot
- Need to cover entire dynamic range - **4 Fixed References.**

Variable Resolution ADC - 25 dB loss

  


- Between two consecutive samples signal changes around 20% - 30%
- Need to cover a portion of entire dynamic range – **Reference Switching**



Variable Resolution ADC - 25 dB loss

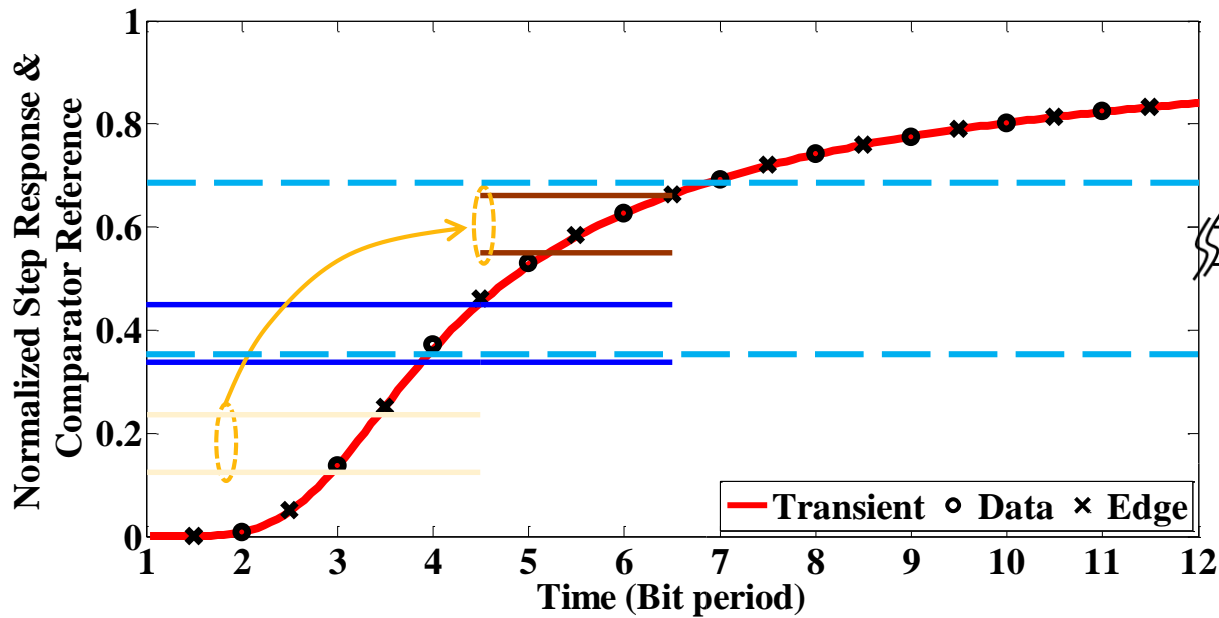

 - Edge comparator output defines **the next probable location of references**




Variable Resolution ADC - 25 dB loss

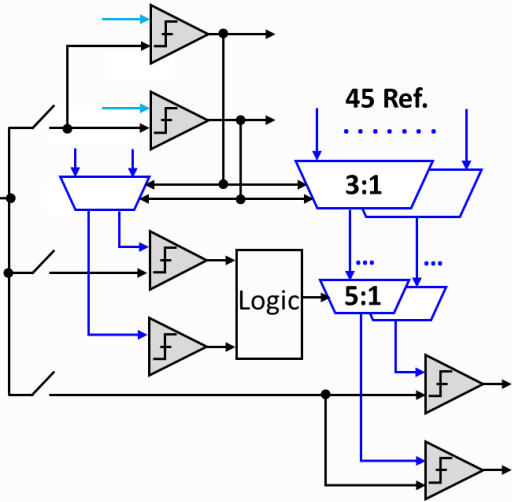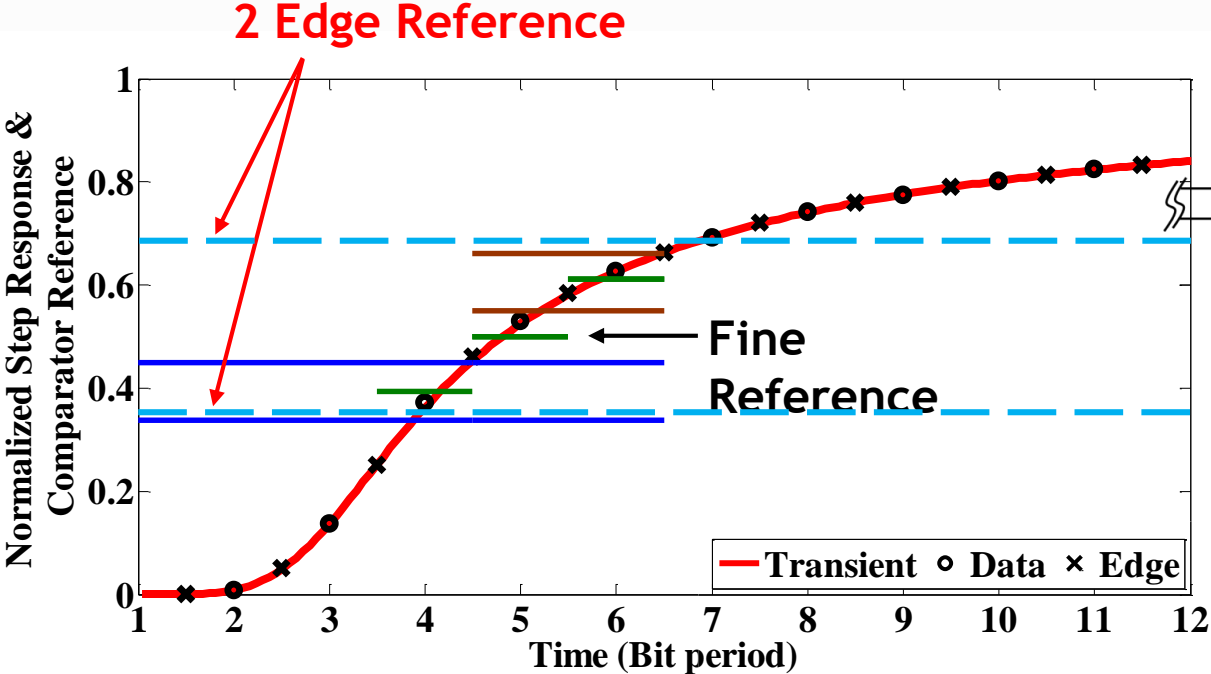


- Fine references are carried over to **the mid of two coarse references**

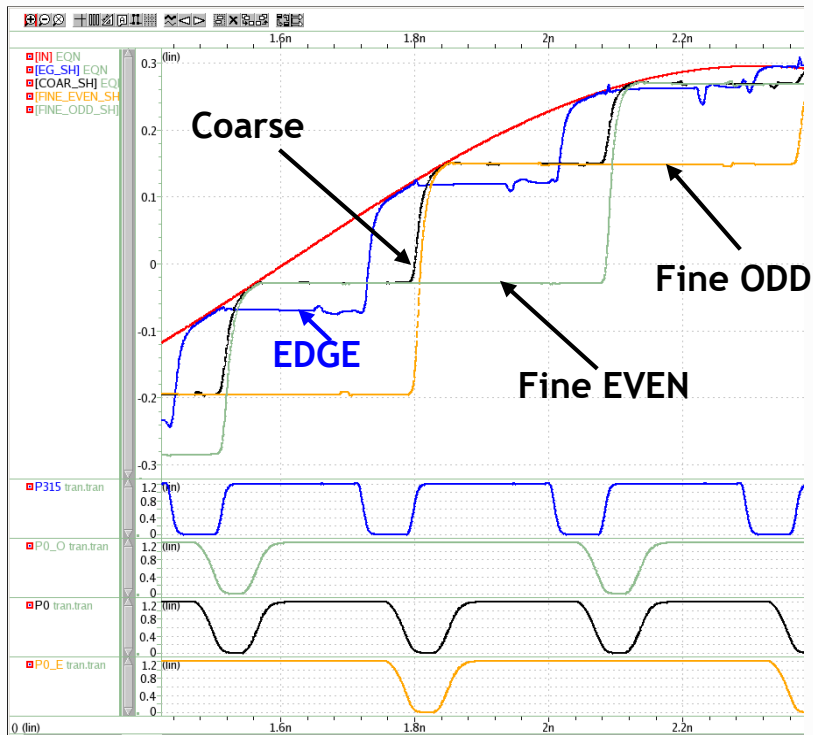Variable Resolution ADC - Sample and Hold





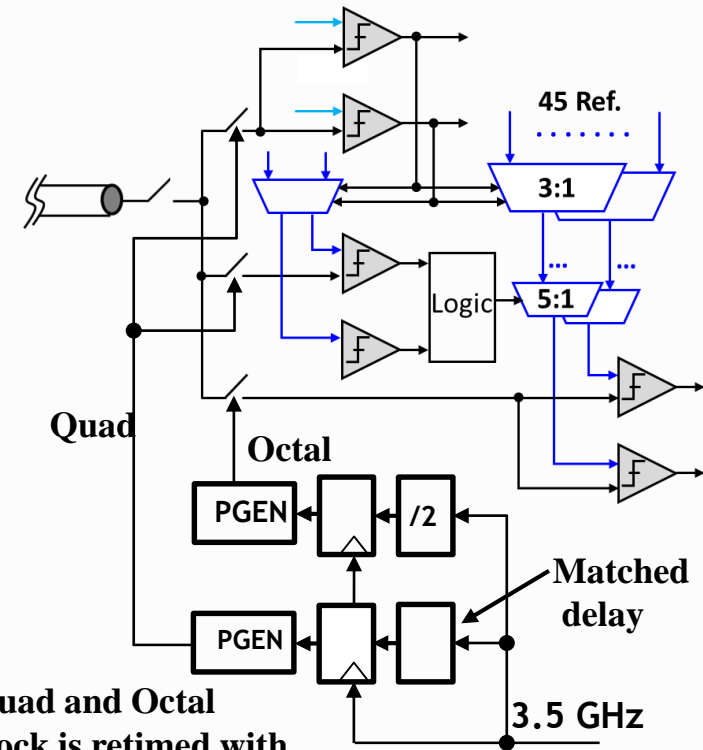Quad Edge
 Octal ODD
 Quad Coarse
 Octal EVEN





- Quad and Octal clock is retimed with a the original quad clock

ADC Offset Correction

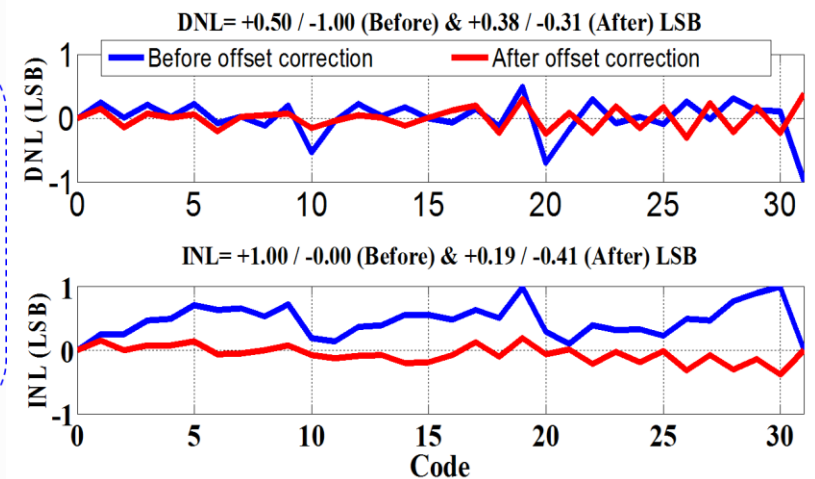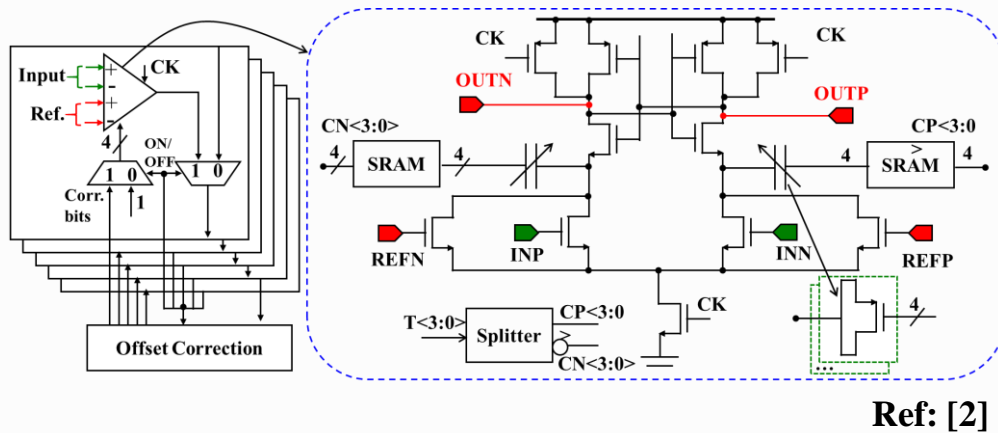


- Unbalance the capacitive load attached to the input of the strong-ARM latch
- Store the bit-decisions into a 6T SRAM to reduce the area.

Measured ADC Performance

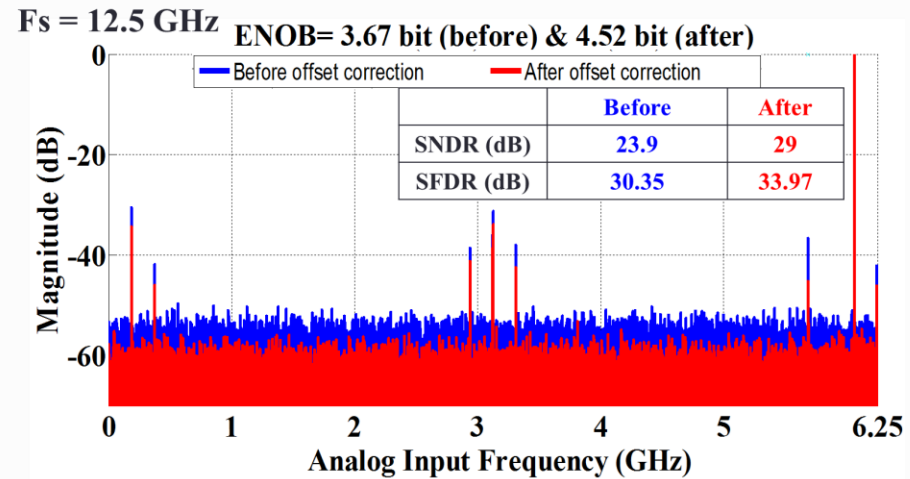 

PAM-4 Digital Receiver Architecture


- Variable Resolution
- Predictive ADC

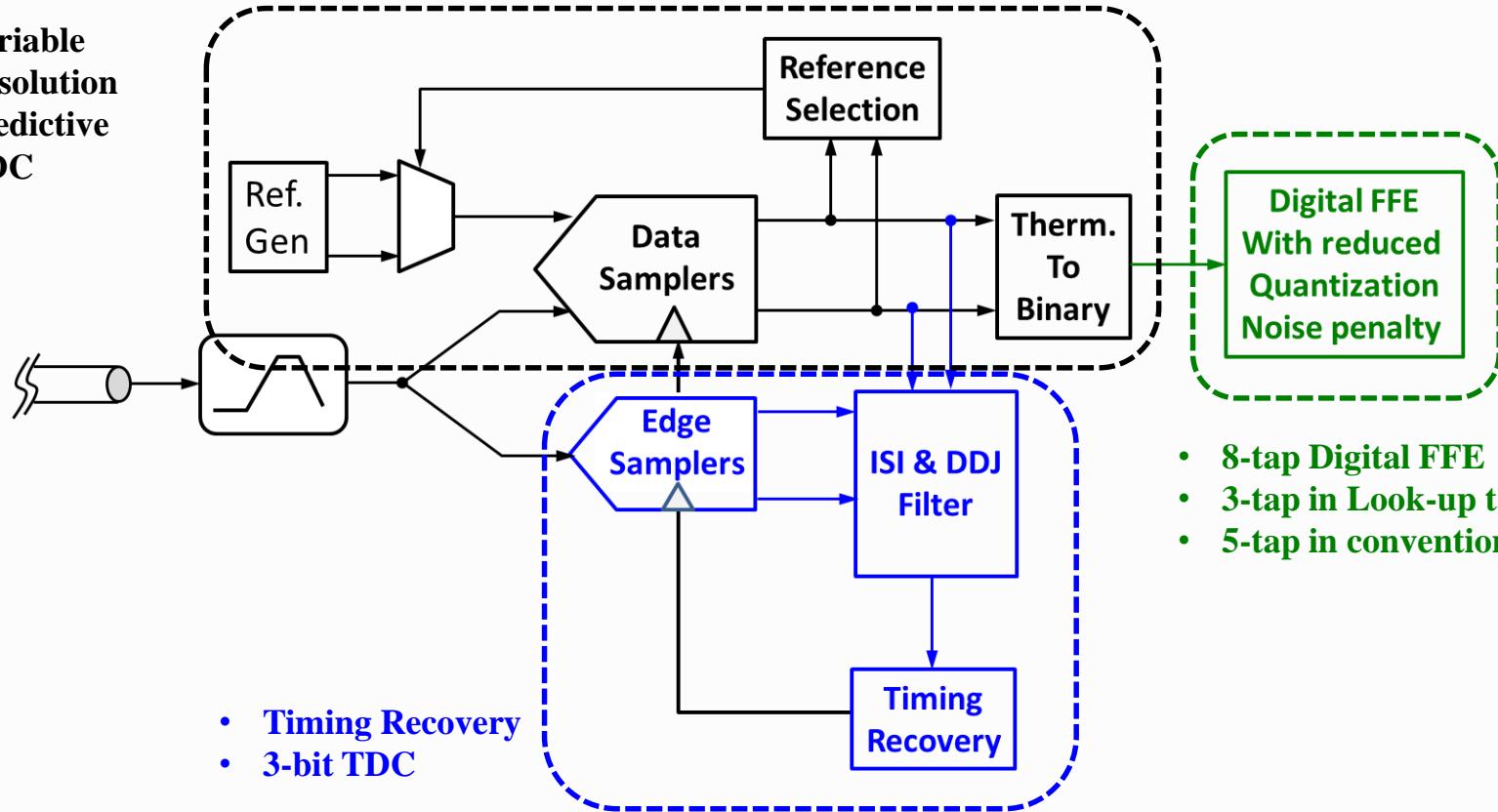

- Timing Recovery
- 3-bit TDC



- 8-tap Digital FFE
- 3-tap in Look-up table
- 5-tap in conventional way

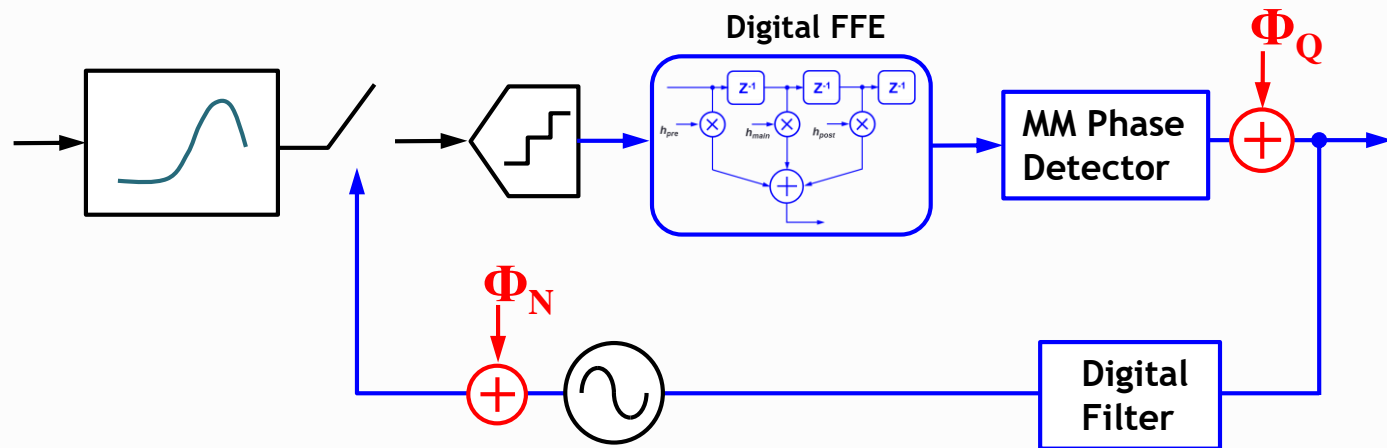Timing Recovery Challenge for ADC-based Receiver



- MM based phase detection is not as robust as 2x (i.e. data and edge) sampled CDR
- Bang-bang or 1 bit phase quantization at the Phase detector increases in-band jitter
- Lowering loop bandwidth increases VCO phase noise contribution
- Loop latency makes it difficult to achieve wider loop bandwidth


Effect of Timing Noise on SNR

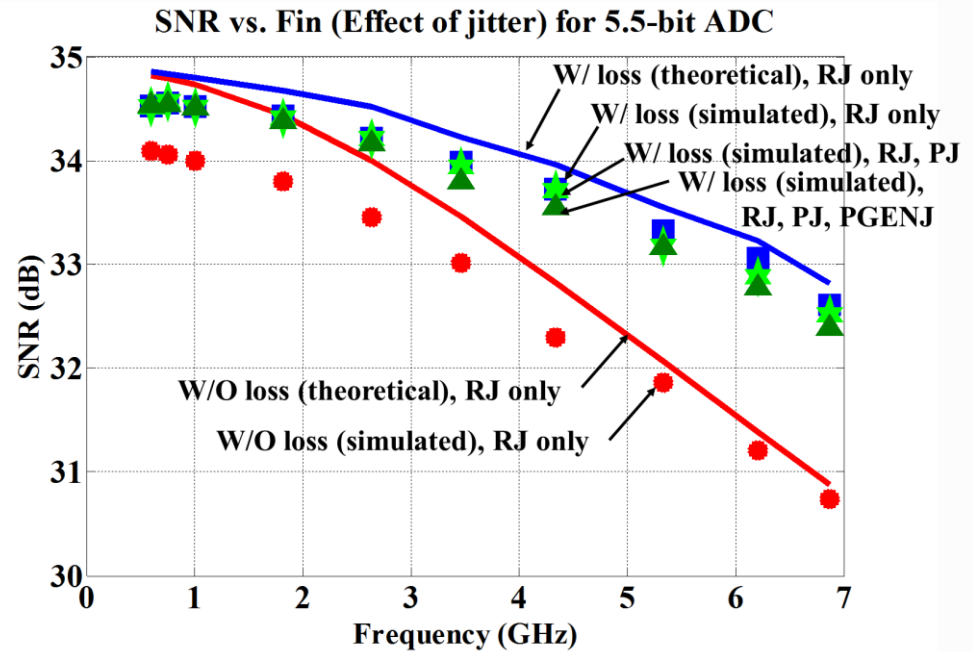 


Effect of timing noise on SNR is less when we consider channel loss!!!

Phase Tracking vs Blind ADC based

[Clifford *et.al.* JSSC, 2013]

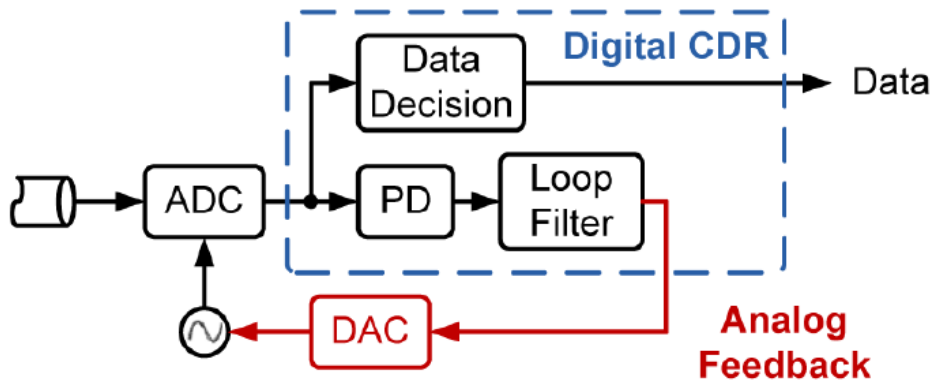


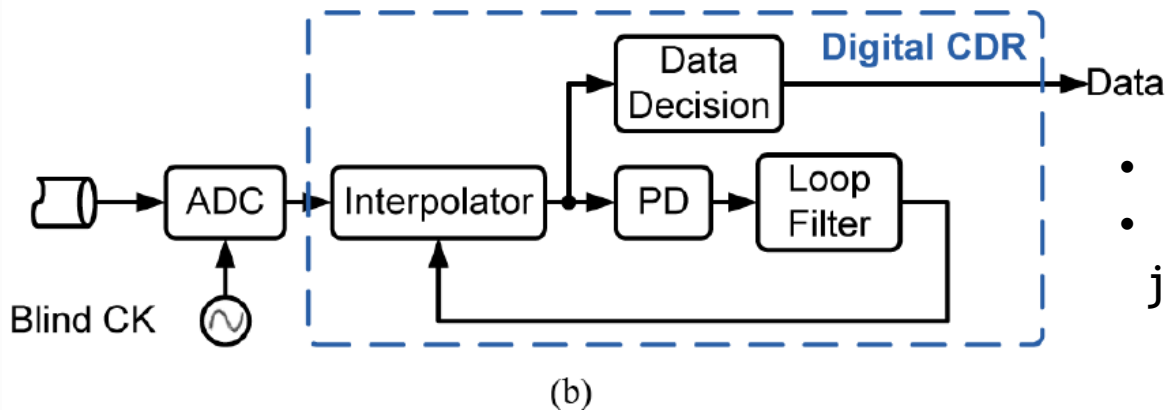- Simple But latency sensitive
- ADC benefits from jitter tracking




- Less latency sensitive
- ADC does not benefits from jitter tracking

Low-latency Timing Recovery

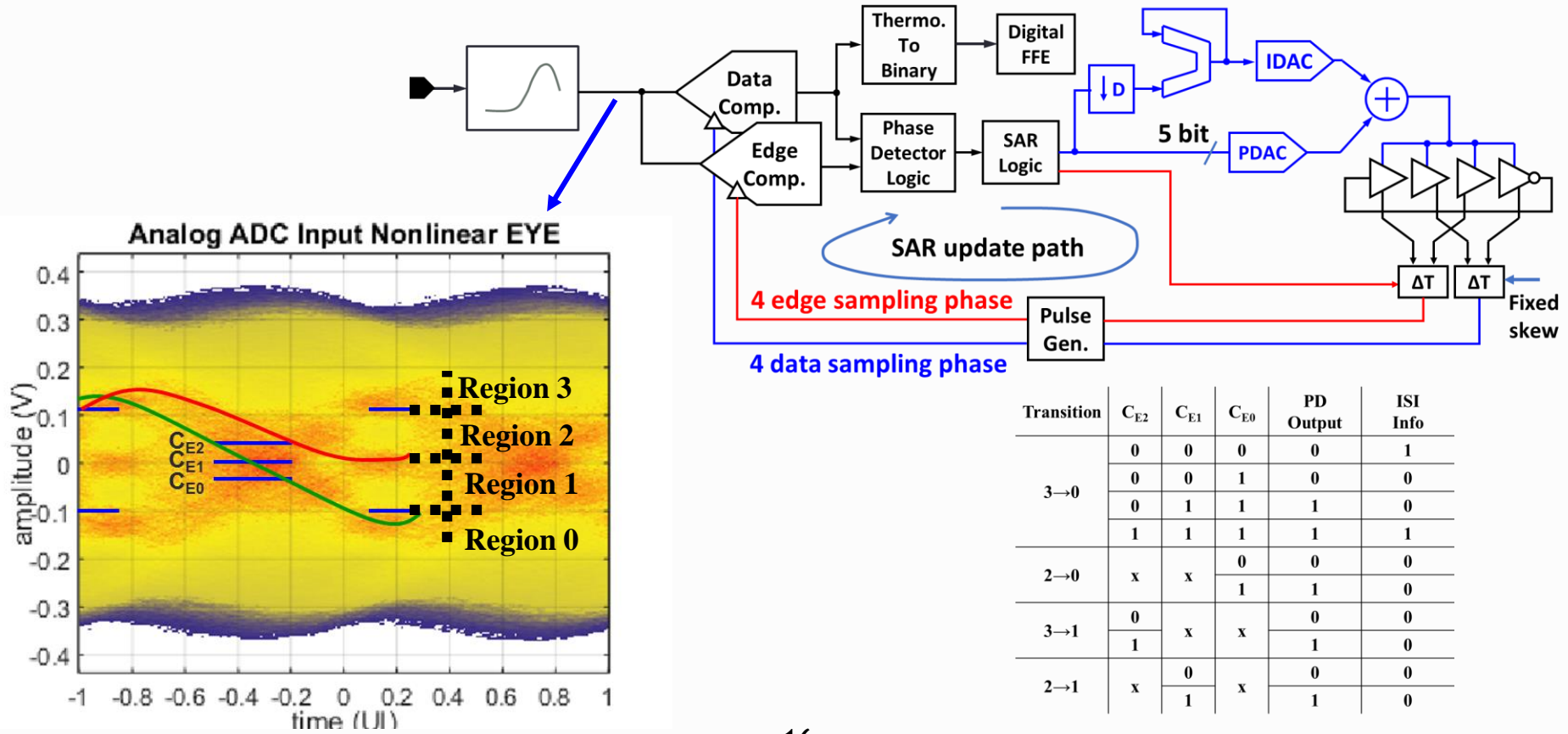

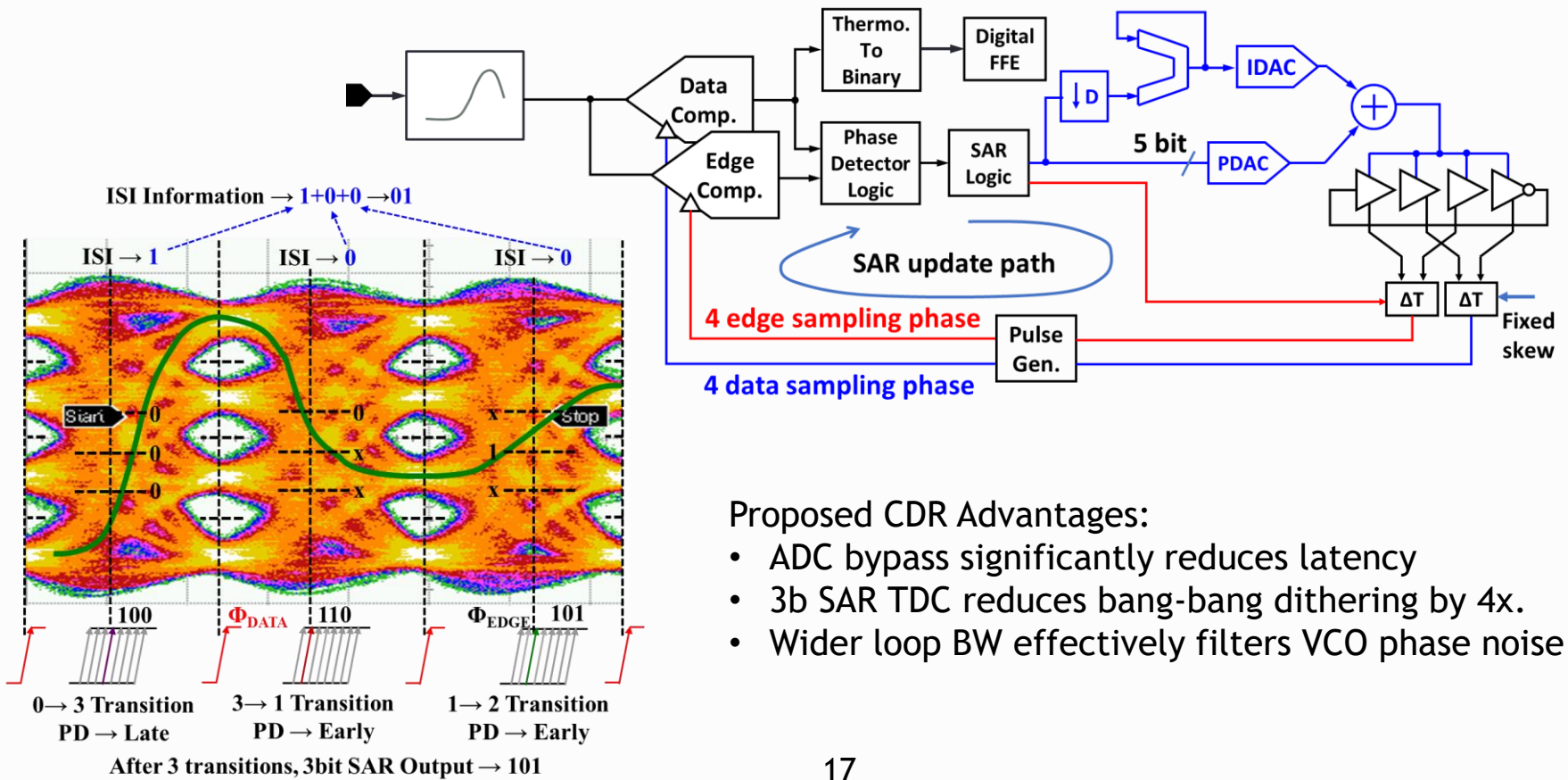Low-latency Timing Recovery - SAR TDC operation




Proposed CDR Advantages:

- ADC bypass significantly reduces latency
- 3b SAR TDC reduces bang-bang dithering by 4x.
- Wider loop BW effectively filters VCO phase noise


CDR Performance

Phase Noise

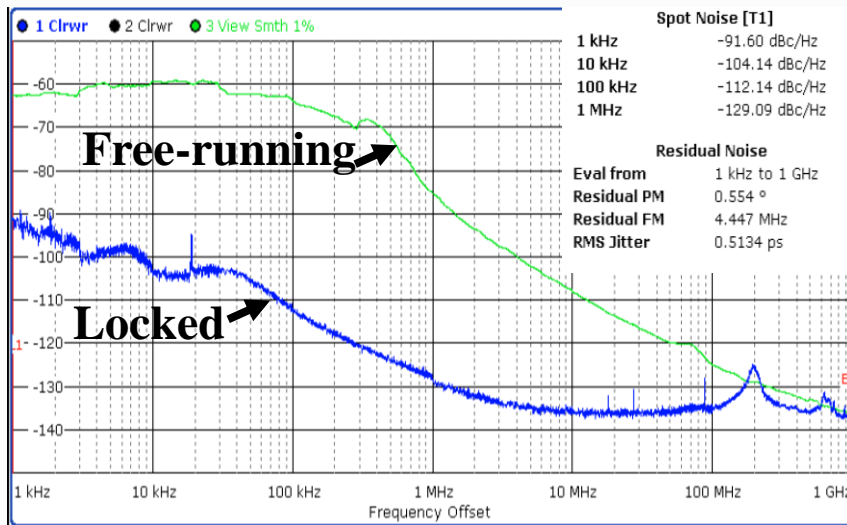


- Integrated jitter = 0.5 ps
- In-band phase noise = -90 dBc/Hz

Jitter Tolerance with 2^7-1 pattern

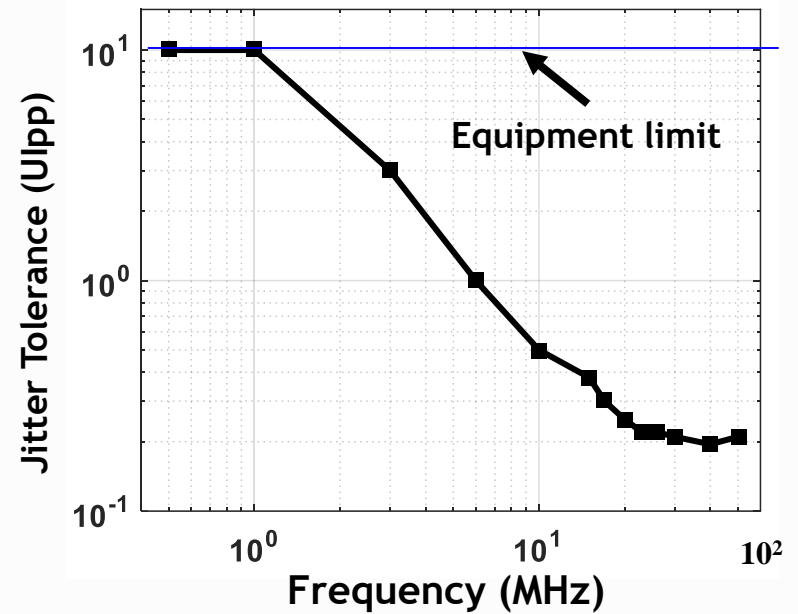


PAM-4 Digital Receiver Architecture

- Variable Resolution
- Predictive ADC

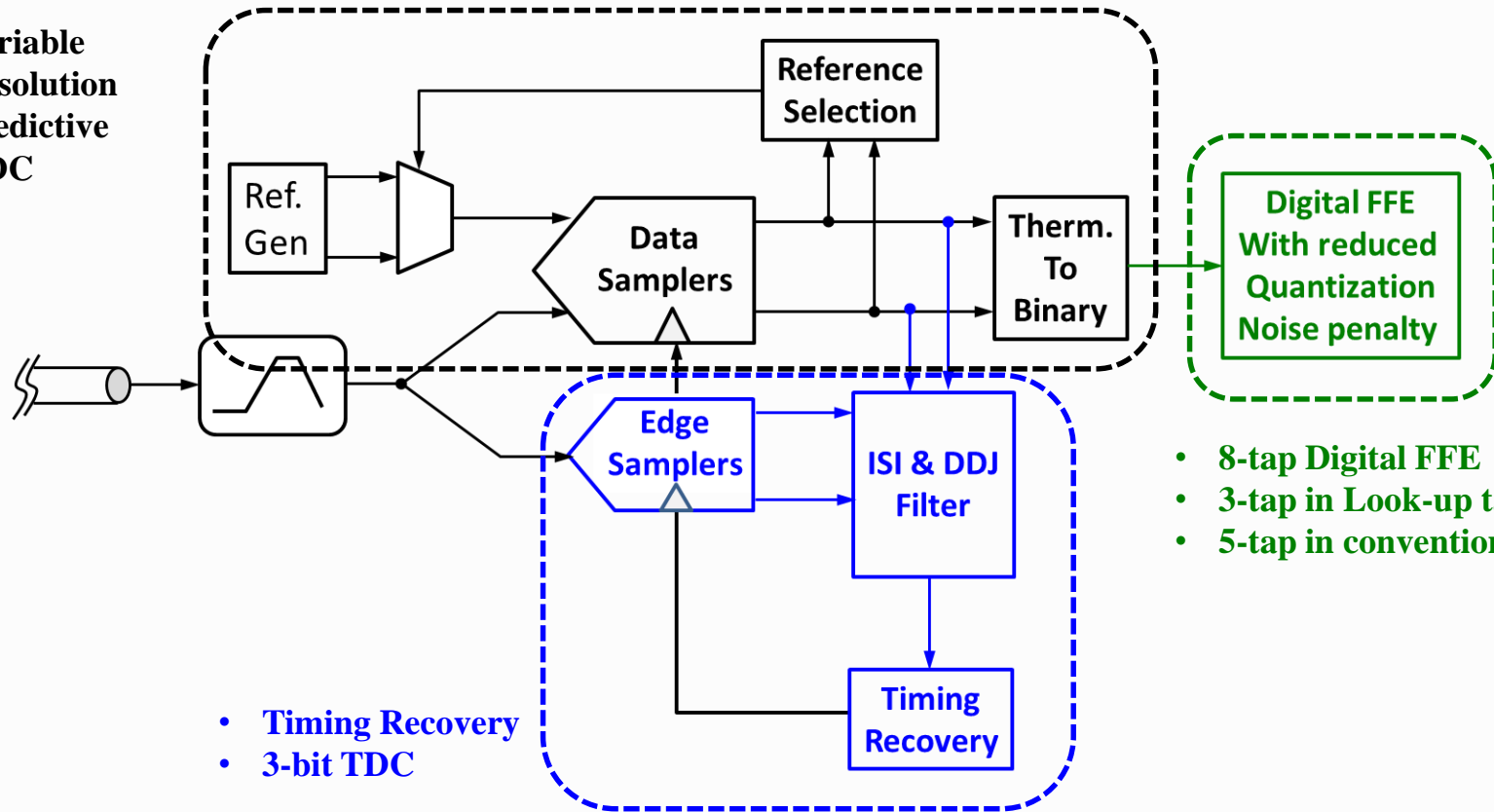

- 8-tap Digital FFE
- 3-tap in Look-up table
- 5-tap in conventional way

Noise Sources in ADC-based Receiver

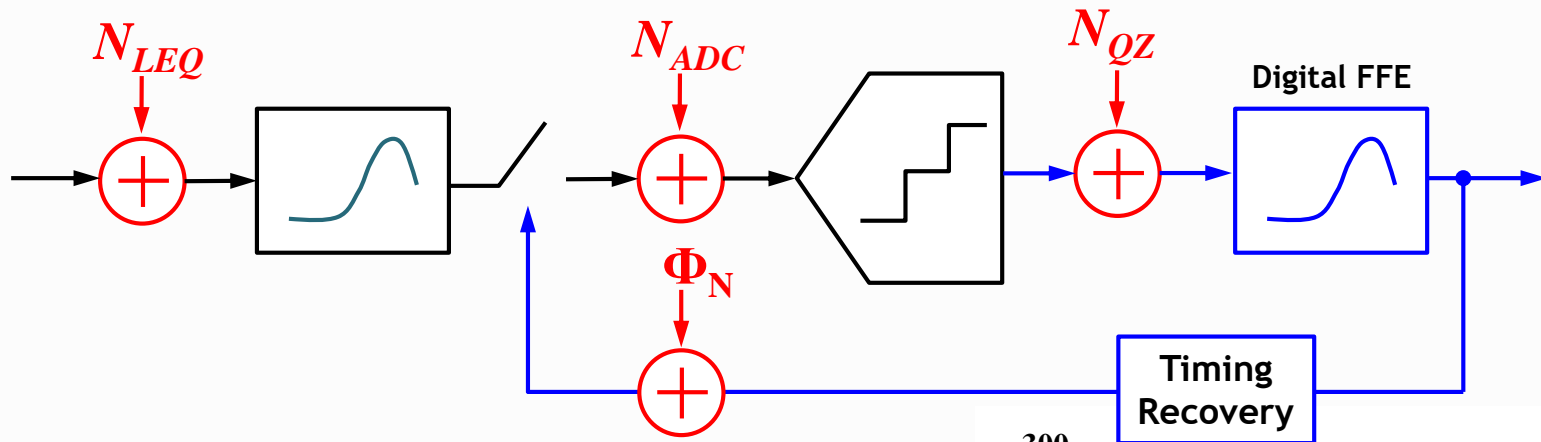

Noise Source

N_{LEQ}

Φ_N

N_{ADC}

N_{QZ}

Constrain

Power/Gain/BW

Power and latency

Power/Settling time

ADC Resolution


Transfer Gain

LEQ + FFE


FFE

FFE

FFE

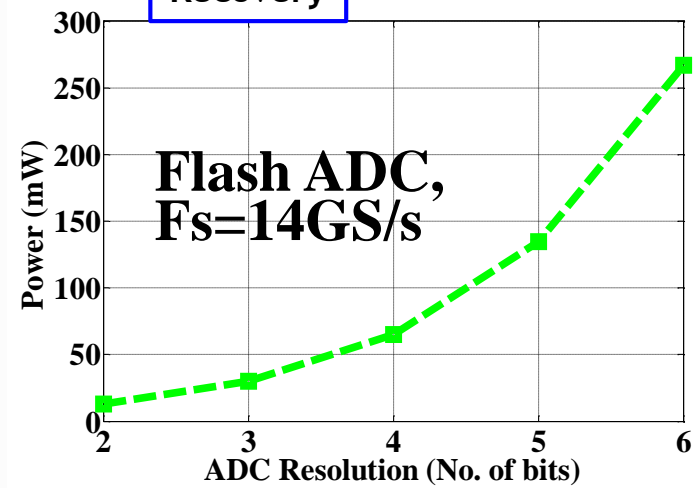


Quantization Noise Impact

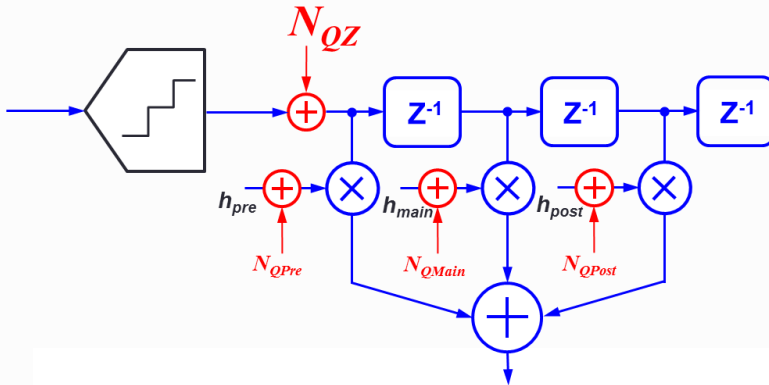


$$N_{QZ,out} = N_{QZ} \cdot |h_{FFE}|^2 + \sqrt{\frac{N^2_{QPre}W^2_{Pre} + N^2_{QMain}W^2_{Main} + N^2_{QPost}W^2_{Post}}{3}}$$

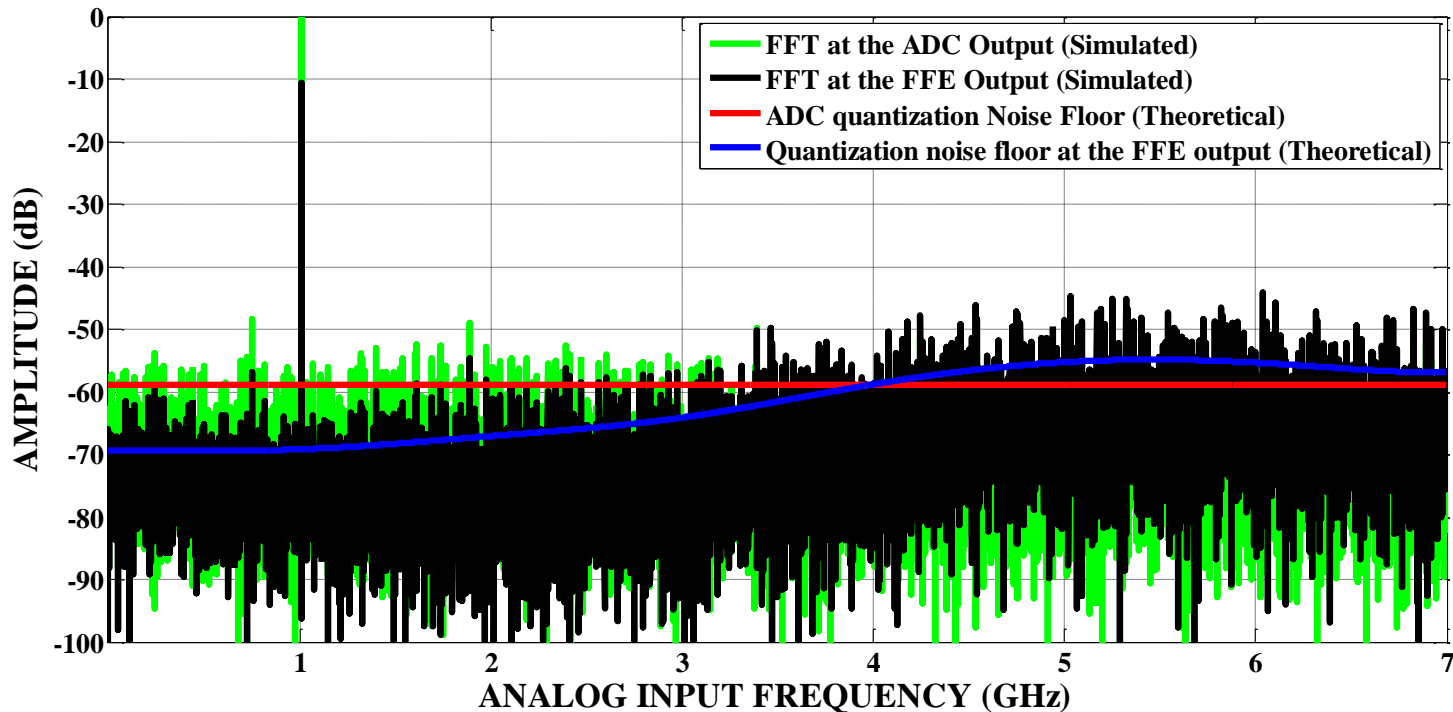
$$W_x = \frac{h_x}{h_{pre} + h_{main} + h_{post}}, \quad x = Pre, Main, Post$$



 How to reduce ADC quantization noise impact?



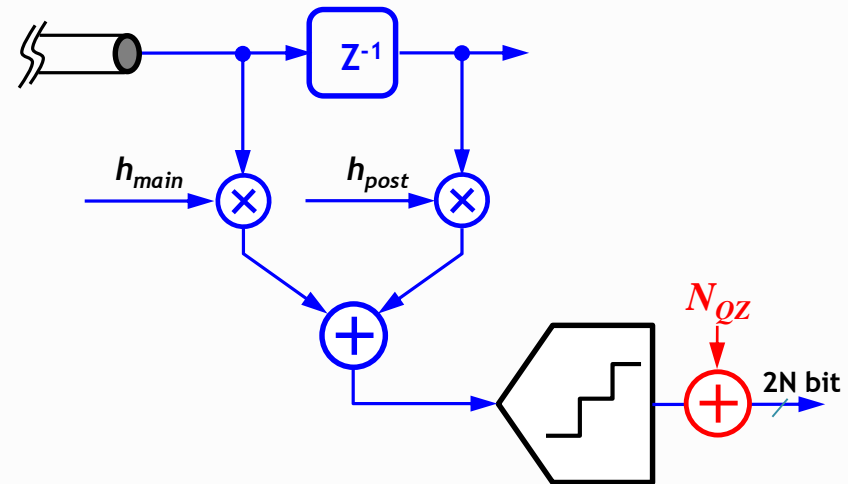
Although Digital FFE output can be 2N bit, we are still limited by ADC's N bit resolution





If FFE can be moved ahead of the ADC than we can Minimize ADC's quantization noise penalty

How can we build a digital FFE with resolution better than the ADC?

Reducing Quantization Noise Impact

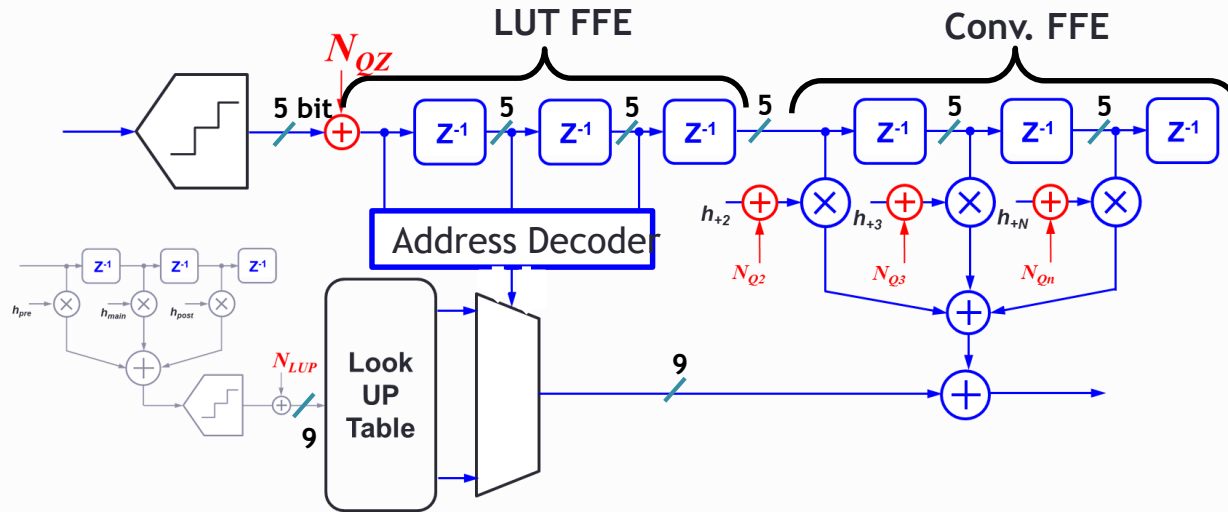


  - LUT based first three taps reduces quantization noise impact
- 3 to 8 taps does not significantly amplify quantization noise




Reducing Quantization Noise Impact

8-tap Conventional

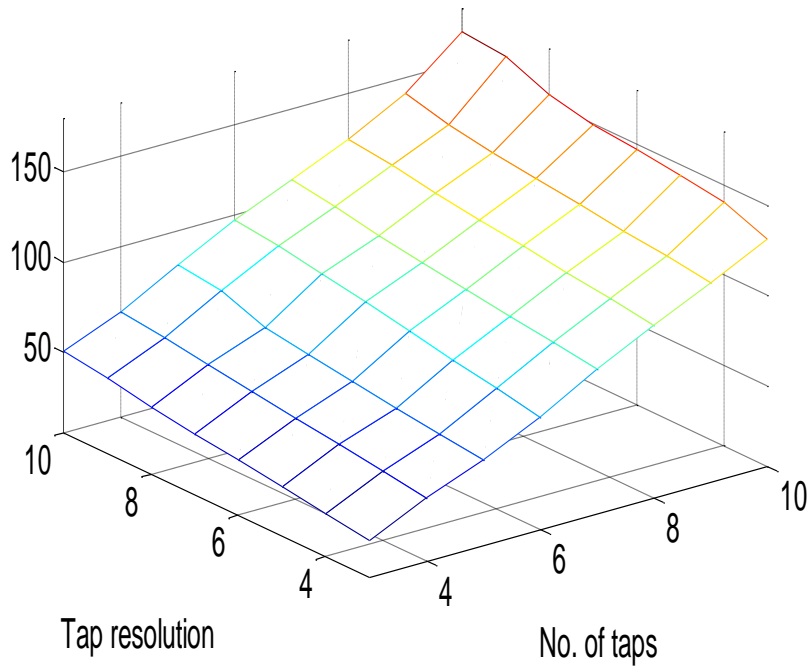

3-tap LUT + 5-tap Conventional

 


Proposed approach is 30% lower power compared to conv. FIR implementation

Area Impact of the proposed solution


8-tap Conventional

500 μm

 


3-tap LUT + 5-tap Conventional



1300 μm

 

 - Area increases by 4x but
 - Standard cell SRAM will reduce is by 25%
 - Area will scale significantly with technology




Implemented Prototype in 65nm CMOS

  

Digital:


- T-to-B, Mode selection
- Retimer

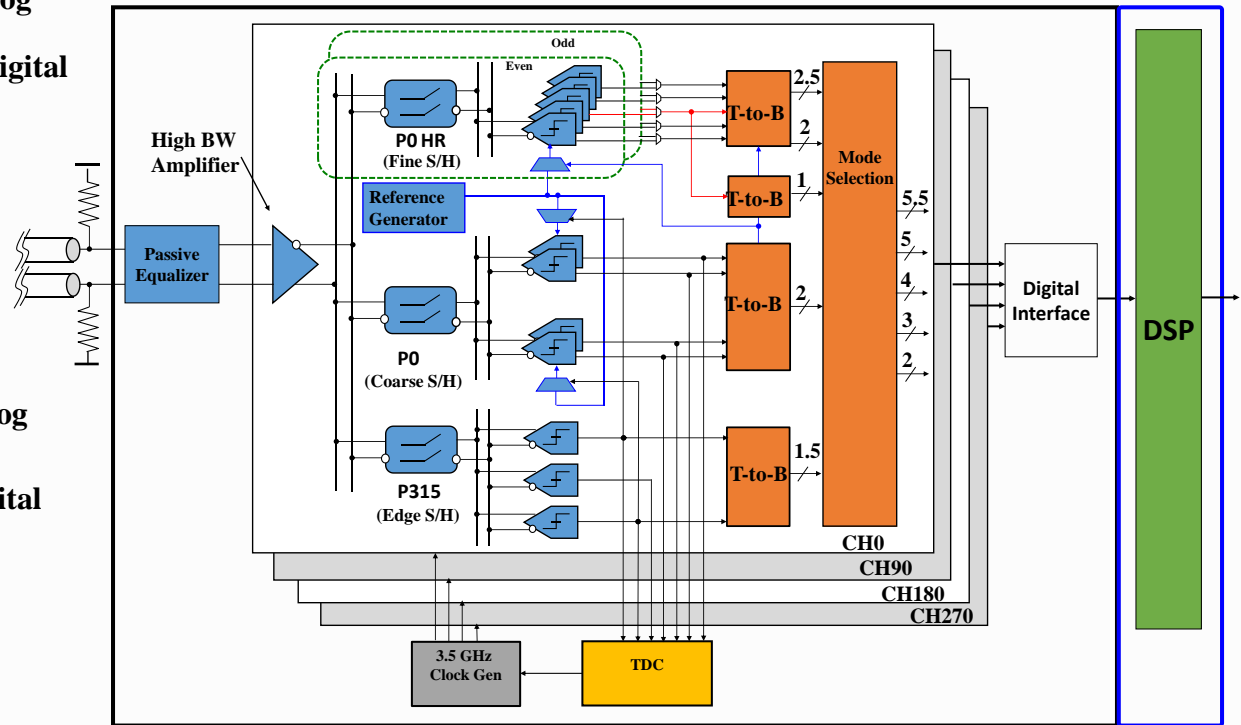

Implemented in TSMC 65nm


FPGA

Implemented Prototype in 65nm CMOS

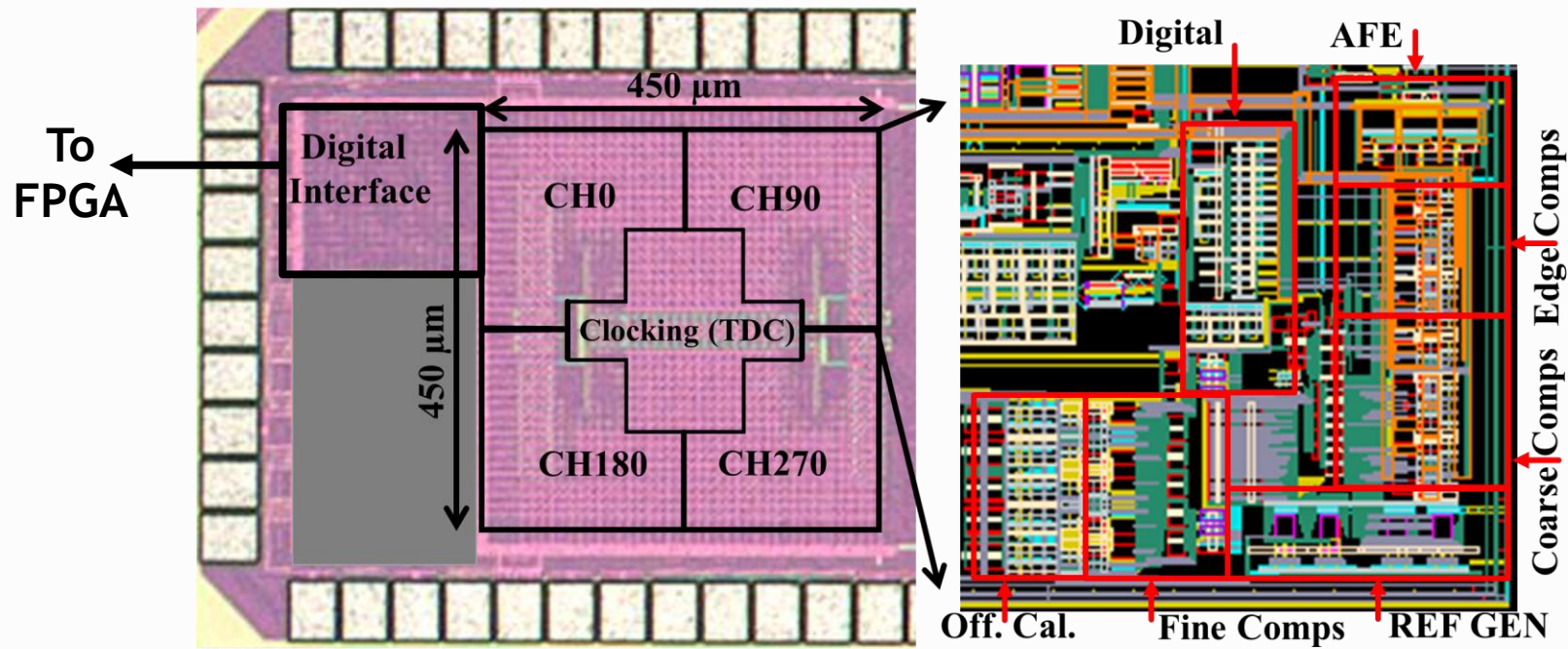

- Heavily digital solution
- Input needs only 7 GHz bandwidth


Experimental Setup

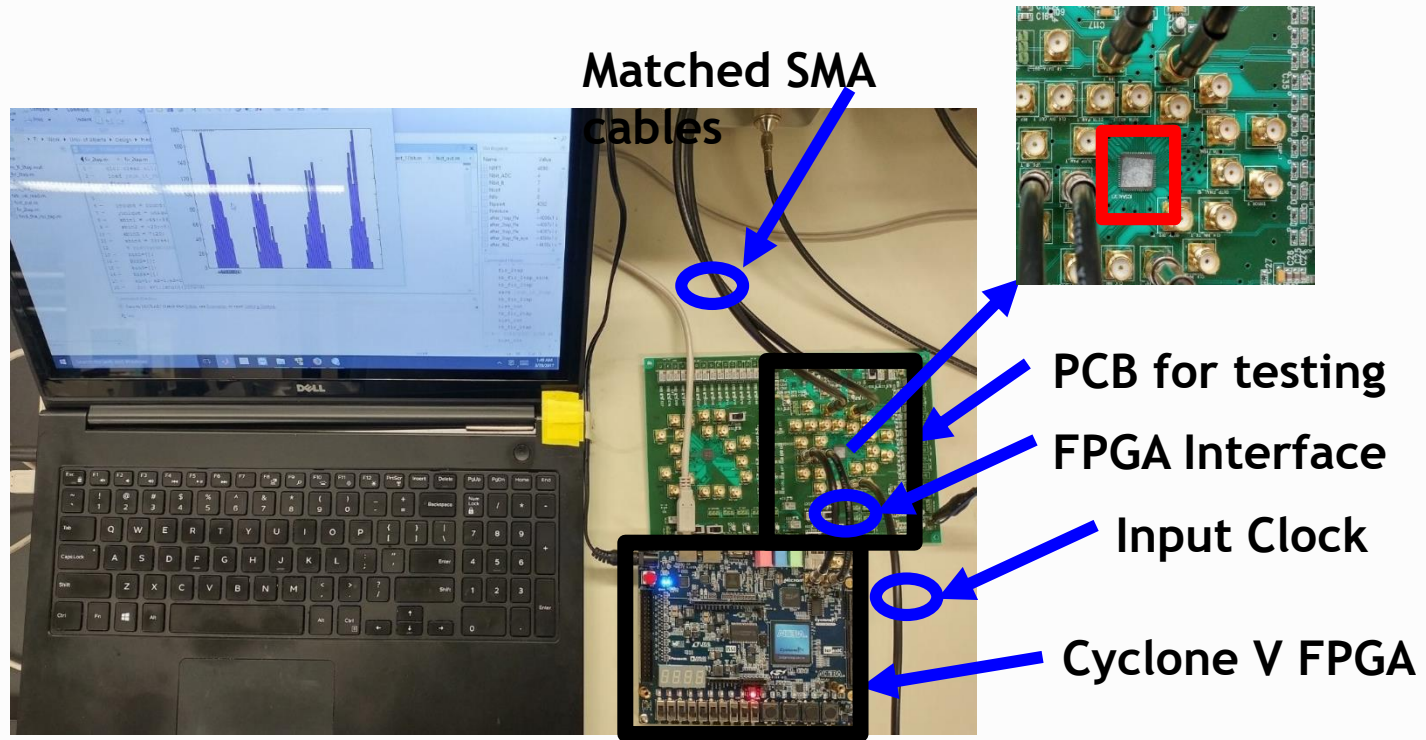

- Varying channel loss by cascading SMA cables.

Input EYE in Digital Domain

 frequency responses
of LR, MR and SR channels




- Tx has **6 dB** equalization
- Linear equalizer boost: **6 to 14 dB**


Linear Equalizer
output EYE

Reconstructed digital
EYE from ADC output


SR

 



MR

 

LR

 



Link Margin at 28Gb/s 30 dB Channel

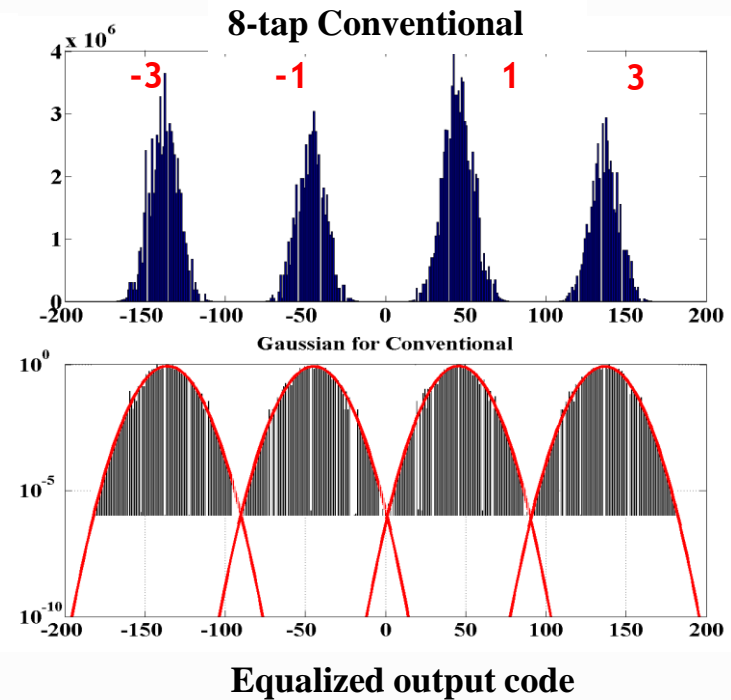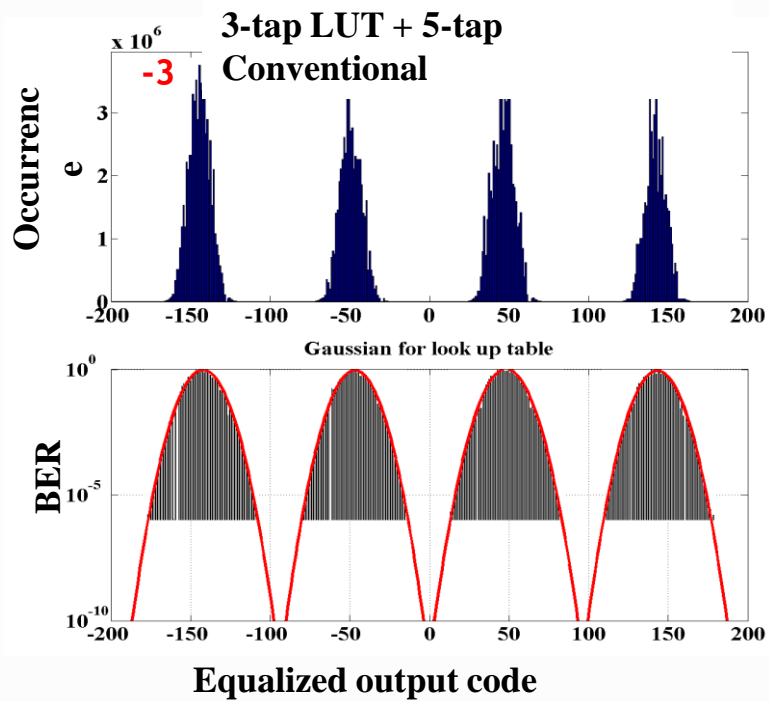

- FPGA gives the distribution of the bins
- The distribution is converted into log-scale 30
- Gaussian fit to extract the BER.

Link Margin Test and Energy Efficiency

Data rate: 28 Gb/s PAM-4

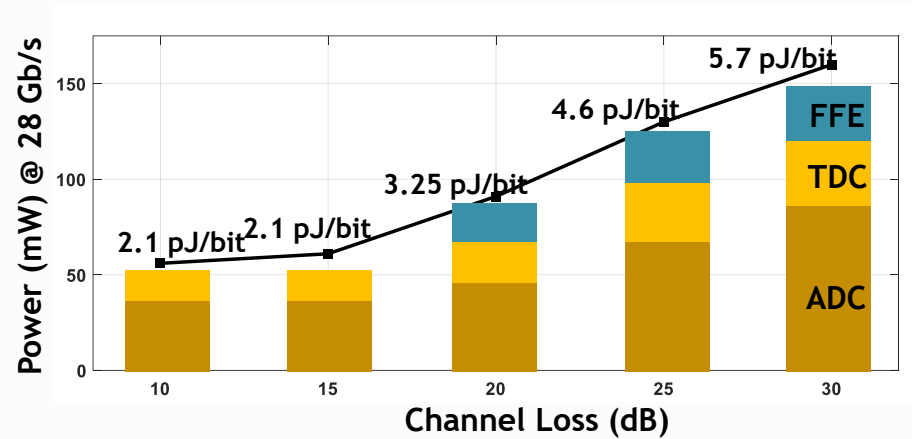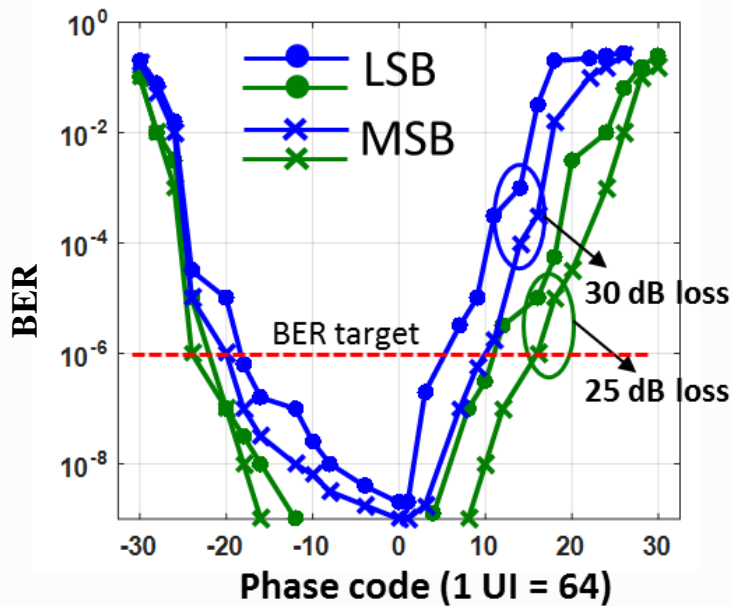

- Receiver can achieve BER up to 10^{-9}

Comparison with state-of-art

	Shafik ISSCC 2015[4]	Frans VLSI 2016[5]	Cui ISSCC 2016[3]	Rylov ISSCC 2016 [6]	This Work
Technology	65 nm CMOS	16 nm FinFET	28 nm CMOS	32 nm CMOS	65 nm CMOS
Data Rate (Gb/s)	10 NRZ	56 PAM-4	32 PAM-4	25 NRZ	28 PAM-4
ADC Architecture	32x TI SAR ADC	32x TI SAR ADC	32x TI SAR ADC	4x Flash ADC	4x Flash ADC
ENOB@ Nyquist	4.74	4.9	5.85	4	4.1
Timing Recovery	N/A	Baud-rate	Baud-rate	Baud-rate	Edge & Data Sampled
Tracking BW	---	---	---	---	10+ MHz
Jitter Tolerance	---	----	---	---	0.2 UIpp @ 50 MHz
Channel Loss Equalization	36.4 dB @ 5 GHz	25 dB @ 14 GHz	32 dB @ 8 GHz	40 dB @ 12 GHz	30 dB @ 7 GHz
Power (mW)	79(w/o DSP) 87(w DSP)	410(w/o DSP)	320	453	130@30 dB } w/o 45 @ 15 dB } DSP 160@30 dB } with 60 @ 15 dB } DSP
FOM (pJ/bit)	8.7	7.32	10	18.12	5.71@ 30 dB } with 2.14@ 15 dB } DSP

Summary of ADC Based Receiver

- ADC- DSP Based receivers are the future for multilevel signaling in advanced CMOS - but it's power has to be reduced.
- DSP needs to be more information efficient - Non-uniform quantization is a simple way to improve effective resolution.
- ADC for wireline is different than general purpose ADC. General purpose ADC considers each sample 'uncorrelated' but in reality channel ISI makes them 'correlated' - predictive ADC is a simple way to take advantage of that.
- Timing recovery is as important as data recovery - Multibit TDC and lower latency is an effective way to improve timing recovery loop and meet jitter requirement of the ADC.